


# COS10004: Computer Systems

## Lab 2

Name: SWH00420 Tran Quoc Dung


Student ID: 103803891

### Part 1: 4-bit adder

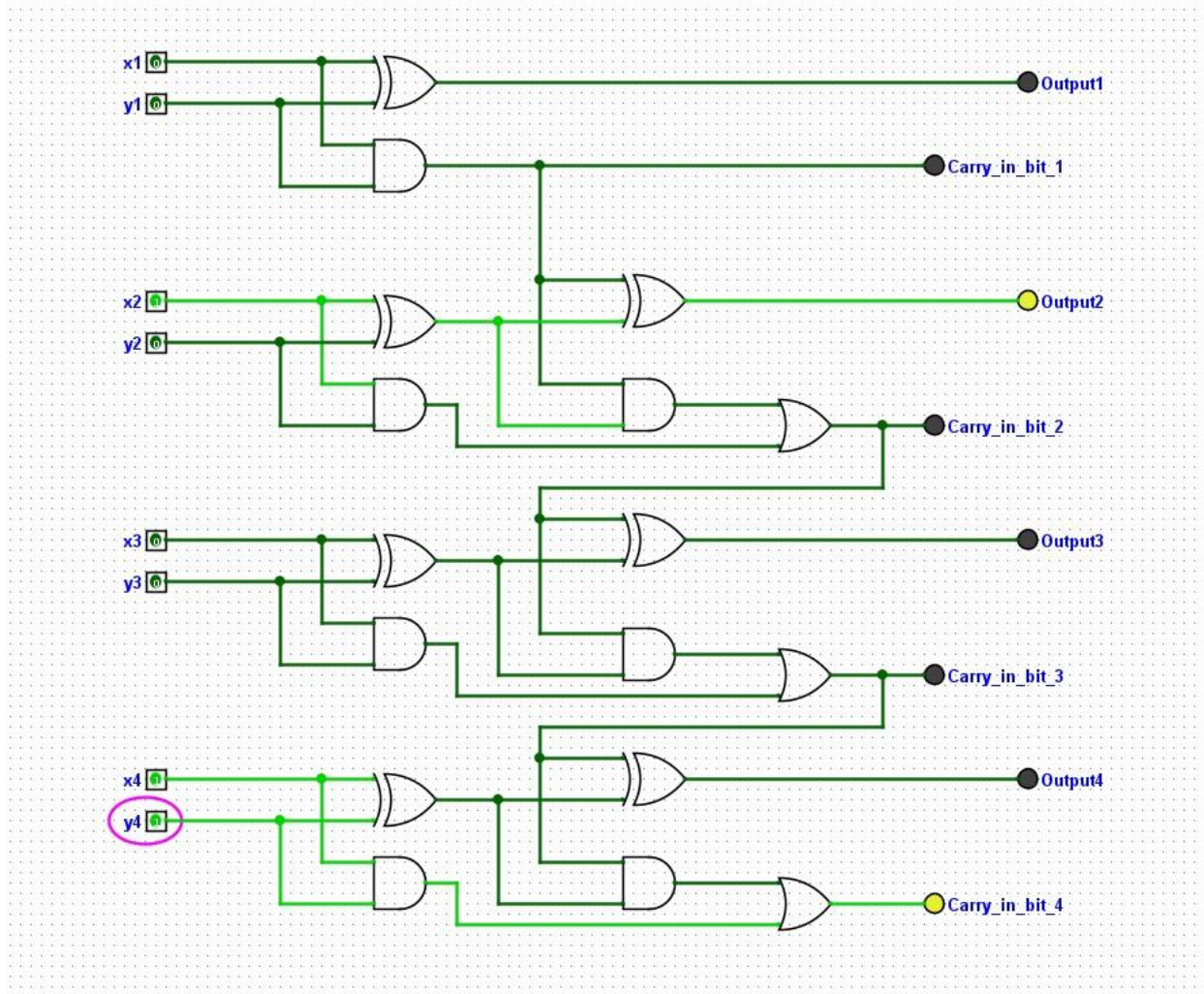

Input A	Input B	Output
0101	0000	0101
0101	0001	0100
0101	0010	0111
0101	0011	0110
0101	0100	0011
0101	0101	0010
0101	0110	0000
0101	0111	0001
0101	1000	1101
0101	1001	1100
0101	1010	1111
0101	1011	1110
0101	1100	1011
0101	1101	1010
0101	1110	1000
0101	1111	1001
 
## **Part 2: Storing bits with Flip Flops**




Set	Reset	Q	Q'
1	0	0	1
1	1	0	0
0	1	1	0
1	1	0	0

11. When one of the inputs is 1, one of the two output LEDs is on simultaneously. This can be used for creating the circuit based on different standards.

12. After setting two inputs to 1, the two LEDs output are turned off. Based on the rules of flip flop, the output should be regarded as the complement of each of them, whereby the circuit will not accept this circumstance.

### Part 3: D Flip Flop

 


Clock	Pin	Q	Q'
0	0	0	0
0	1	0	0
1	1	0	1
1	0	1	0

15. There is only 1 input in the D Flip Flop, which will have the same value with Q if the clock in the circuit goes active.

16. The clock helps evaluate and determine the signal provided in the circuit. To elaborate, when the signal determined by the clock is high, the inputs become active and the reverse situation.

17. D Flip Flop is more preferred since it does not require extra pins from designers to convert from serial to parallel like R-S Flip Flop.

### Part 4: J-K Flip Flops

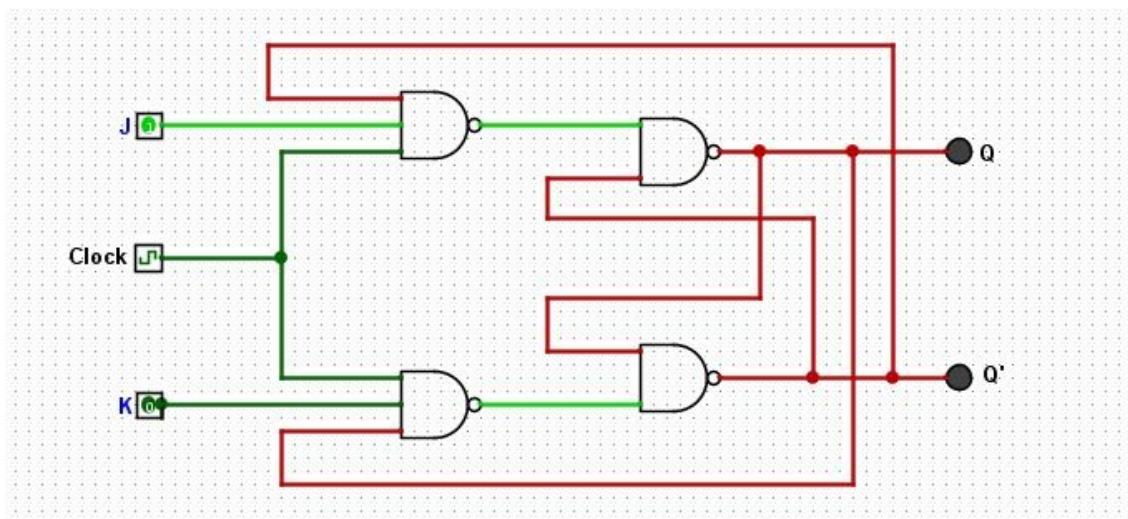

<b>J</b>	<b>K</b>	<b>Q (when clocked)</b>	<b>Q' (when clocked)</b>
0	0	0	0
0	1	0	0
1	0	0	0
1	1	0	0

20. The J-K Flip Flop will require a NOT gate to generate like the D Flip Flop

21. J and K inputs have to be both “1”